

Problem 1

My student ID's last 3 digits are 102.

$$\text{So, } x = 1 + 0 + 2 = 3 = \text{odd}$$

So, the BJT model is BC548.

From data sheet,

$$I_C = 2 \text{ mA}$$

$$V_{CE} = 5 \text{ V}$$

$$V_{CC} = 10 \text{ V}$$

$$\beta = 110 (\text{min})$$

Now,

$$V_E = \frac{1}{10} V_{CC} = \frac{1}{10} \times 10 \text{ V} = 1 \text{ V}$$

$$R_E = \frac{V_E}{I_E} \approx \frac{V_E}{I_C} = \frac{1 \text{ V}}{2 \text{ mA}} = 500 \Omega$$

$$R_C = \frac{V_{RC}}{I_C} = \frac{V_{CC} - V_{CE} - V_E}{I_C} = \frac{(10 - 5 - 1) \text{ V}}{2 \text{ mA}} = 2 \text{ k}\Omega$$

$$V_B = V_{BE} + V_E = 0.7 \text{ V} + 1 \text{ V} = 1.7 \text{ V}$$

$$R_2 \leq \beta R_E$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$R_2 \leq \frac{1}{10} (110) \times (0.5 \text{ k}\Omega) = 5.5 \text{ k}\Omega$$

Here,

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} \Rightarrow 1.7 \text{ V} = \frac{(5.5 \Omega)(10 \text{ V})}{R_1 + 5.5 \text{ k}\Omega}$$


$$\therefore R_1 = 26.85 \text{ k}\Omega$$

$$\text{So, } R_1 = 26.85 \text{ k}\Omega$$

$$R_2 = 5.5 \text{ k}\Omega$$

$$R_C = 2 \text{ k}\Omega$$

$$R_E = 500 \Omega$$

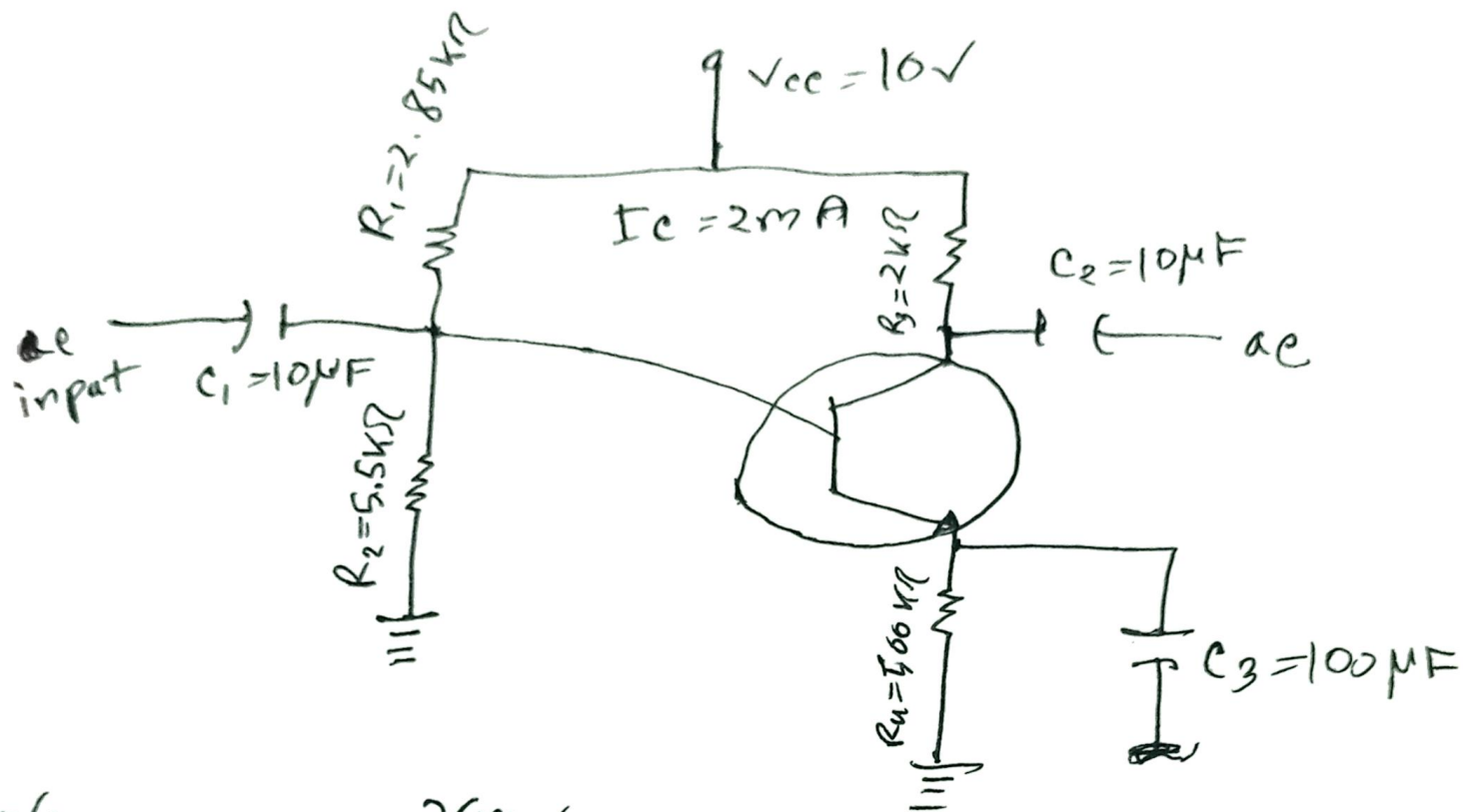

$$\text{Now, } r_c = \frac{26mV}{I_E} \approx \frac{26mV}{I_C} = \frac{26mV}{2mA} = 13\Omega$$

Input impedance, $Z_{in} = R_1 \parallel R_2 \parallel \beta r_E$

$$= \left(\frac{1}{26.85} + \frac{1}{5.5} + \frac{1}{110 \times 13 \times 10^{-3}} \right)^{-1}$$

$$= 1.089 k\Omega$$

Out put impedance Z_{out}

$$= R_C \parallel R_o$$

$$= \left(\frac{1}{R_C} + \frac{1}{R_o} \right)^{-1}$$

$$= \left(\frac{1}{R_C} + \frac{1}{\infty} \right)^{-1}$$

$$= R_C$$

$$= 2 \text{ k}\Omega$$


$$\text{Input AC } V = \left(\frac{\cancel{1} + 0 + 2}{3} \right) V$$

$$= 1 V$$


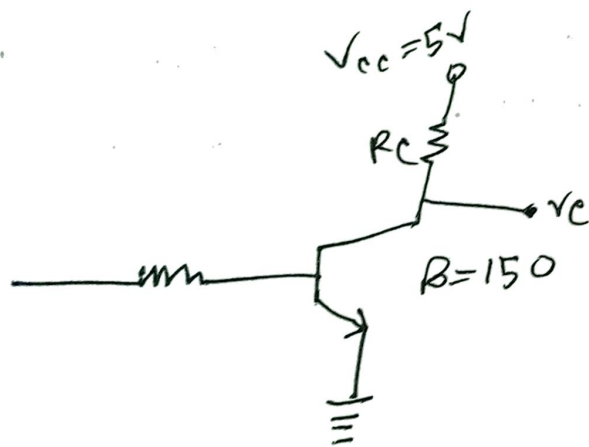
Problem-2:

The sum of my student ID's last 3 digits are $1+0+2 = 3 = \text{odd}$. So, I am going to design a 5V relay module circuit using the SRD-05VDC-SL-C relay.

From Datasheet, $I_{C \text{ SAT}} = 89.3 \text{ mA}$



$$\beta = 150$$

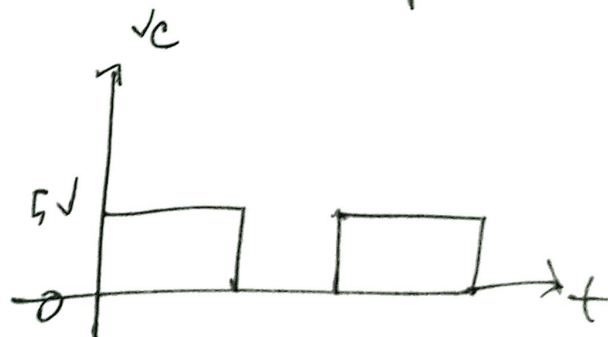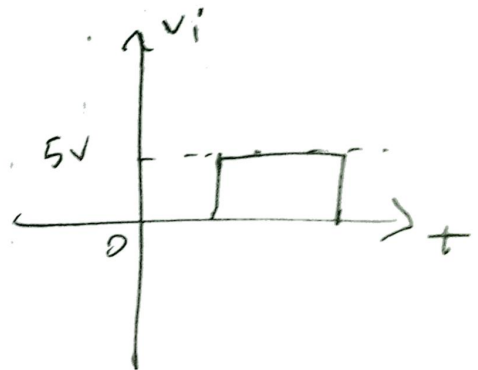

$$I_B > \frac{I_{CSAT}}{\beta}$$

$$\Rightarrow I_B > \frac{89.3 \text{ mA}}{150}$$

$$\therefore I_B = 0.595 \text{ mA}$$

$$\text{Let, } I_B = 0.6 \text{ mA}$$

$$\therefore R_B = \frac{5 - 0.7}{0.6}$$

$$= 7.167 \text{ k}\Omega$$

